

Adder

Adder

- **Review 01_numbers.ppt**

اعمال ریاضی باینری: جمع

• قوانین: مانند جمع دسیمال

• با این تفاوت که $1+1 = 10$ ← تولید نقلی

$$\begin{array}{r}
 \overset{+1}{1} \overset{+1}{0} \overset{+1}{1} \overset{+1}{1} \overset{+1}{0} \overset{+1}{1} \\
 + \quad 0 \ 1 \ 1 \ 0 \ 0 \ 1 \\
 \hline
 1 \ 0 \ 0 \ 0 \ 1 \ 1 \ 0
 \end{array}$$

$0+0 = 0c0$ (sum 0 with carry 0) ↙

$0+1 = 1+0 = 1c0$ ↙

$1+1 = 0c1$ ↙

$1+1+1 = 1c1$ ↙

Carry	1	1	1	1	1	0
Augend	0	0	1	0	0	1
Addend	0	1	1	1	1	1
Result	1	0	1	0	0	0

نمایش اعداد

$$N^* = 2^n - N$$

Example: Twos complement of 7

$$\begin{array}{r} 2^4 = 10000 \\ \text{sub } 7 = \underline{0111} \\ 1001 = \text{repr. of } -7 \end{array}$$

مکمل 2:

Example: Twos complement of -7

$$\begin{array}{r} 2^4 = 10000 \\ \text{sub } -7 = \underline{1001} \\ 0111 = \text{repr. of } 7 \end{array}$$

Shortcut method:

Twos complement = bitwise complement + 1

0111 -> 1000 + 1 -> 1001 (representation of -7)

1001 -> 0110 + 1 -> 0111 (representation of 7)

جمع و تفریق مکمل 2

If
(carry-in to sign = carry-out)
then ignore carry

if
(carry-in \neq carry-out)
then overflow

$$\begin{array}{r} 4 \quad 0100 \\ + 3 \quad 0011 \\ \hline 7 \quad 0111 \end{array}$$

$$\begin{array}{r} -4 \quad 1100 \\ + (-3) \quad 1101 \\ \hline -7 \quad 11001 \end{array}$$

$$\begin{array}{r} 4 \quad 0100 \\ - 3 \quad 1101 \\ \hline 1 \quad 10001 \end{array}$$



$$\begin{array}{r} -4 \quad 1100 \\ + 3 \quad 0011 \\ \hline -1 \quad 1111 \end{array}$$

Simpler addition scheme makes twos complement the most common choice for integer number systems within digital systems

Overflow Conditions

سریز

  Add two positive numbers to get a negative number
or two negative numbers to get a positive number



سریز

Overflow Conditions

$$\begin{array}{r} 5 \quad \quad 0111 \\ \quad \quad 0101 \\ \hline 3 \quad \quad 0011 \\ -8 \quad \quad 1000 \end{array}$$

Overflow

$$\begin{array}{r} 5 \quad \quad 0000 \\ \quad \quad 0101 \\ \hline 2 \quad \quad 0010 \\ 7 \quad \quad 0111 \end{array}$$

No overflow

$$\begin{array}{r} -7 \quad \quad 1000 \\ \quad \quad 1001 \\ \hline -2 \quad \quad 1100 \\ 7 \quad \quad 10111 \end{array}$$

Overflow

$$\begin{array}{r} -3 \quad \quad 1111 \\ \quad \quad 1101 \\ \hline -5 \quad \quad 1011 \\ -8 \quad \quad 11000 \end{array}$$

No overflow

Overflow when carry in to sign \neq carry out

Half Adder (HA)

➤ Add single bits


A _i	B _i	Sum	Carry
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

A _i \ B _i	0	1
0	0	1
1	1	0

A _i \ B _i	0	1
0	0	0
1	0	1


$$\begin{aligned}\text{Sum} &= \bar{A}_i B_i + A_i \bar{B}_i \\ &= A_i \oplus B_i\end{aligned}$$

$$\text{Carry} = A_i \cdot B_i$$

 

Full Adder

- Add multiple bits

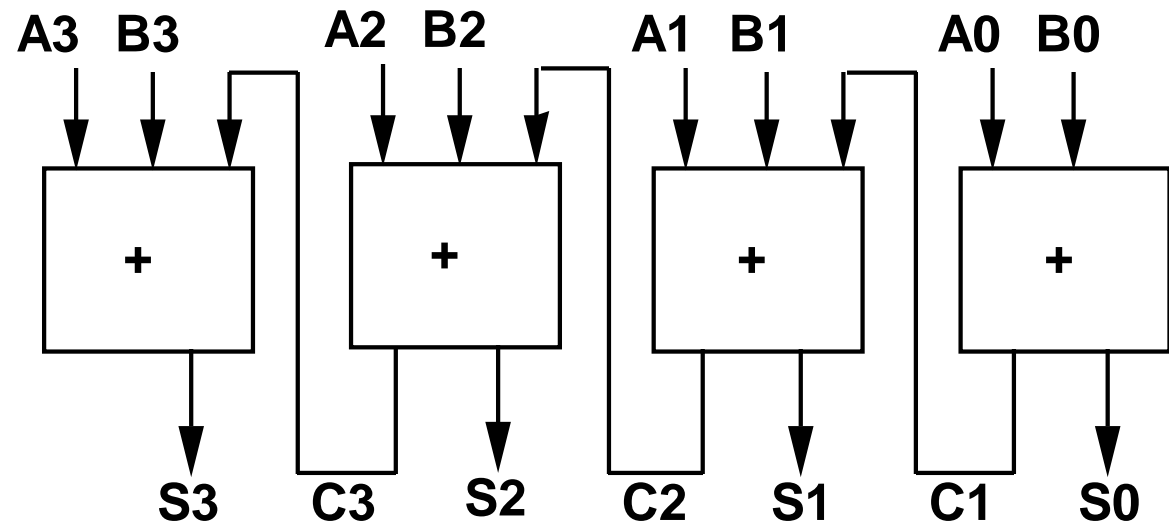

Full Adder (FA)

A	B	C _i	S	C _o
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

$$S = C_i \text{ xor } A \text{ xor } B$$



$$C_o = B C_i + A C_i + A B = C_i (A + B) + A B$$

S

C _i	A B			
	00	01	11	10
0	0	1	0	1
1	1	0	1	0


C_o

C _i	A B			
	00	01	11	10
0	0	0	1	0
1	0	1	1	1

 
 


Full Adder Using 2 Half Adders

 
- A full adder can also be realized with two half adders and an OR gate, since C_{i+1} can also be expressed as:
- $C_{i+1} = A_i B_i + (A_i \oplus B_i) C_i$
and $S_i = (A_i \oplus B_i) \oplus C_i$





Example: 4-bit Ripple Carry Adder

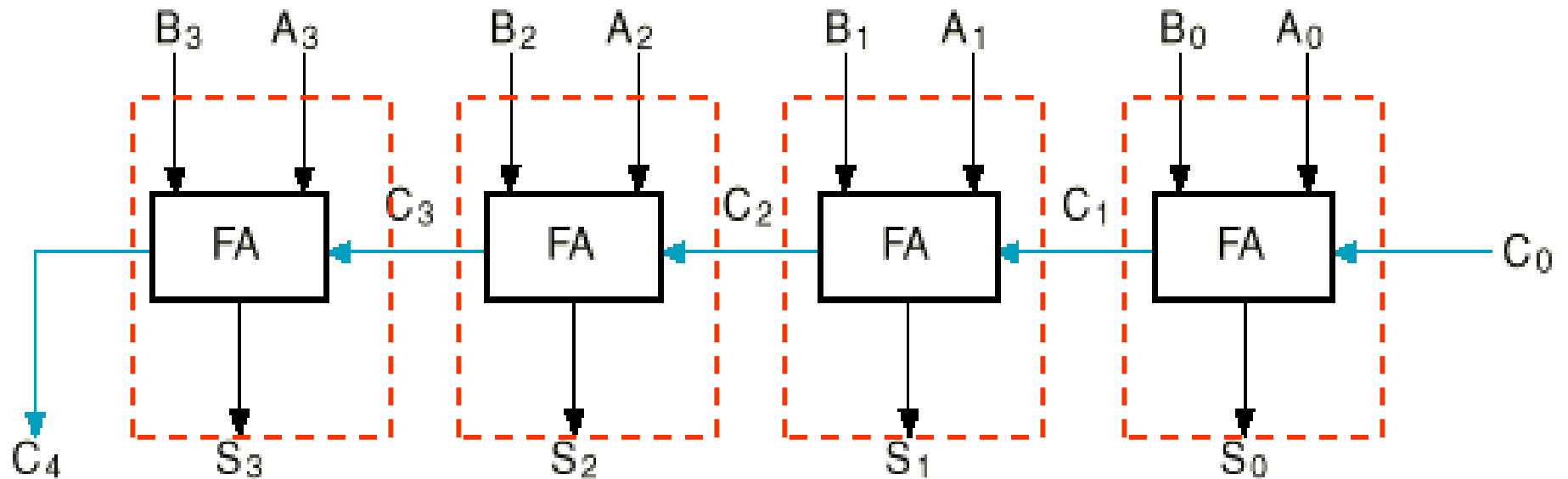 

Delay Analysis of Ripple Adder

 

4 stage adder

 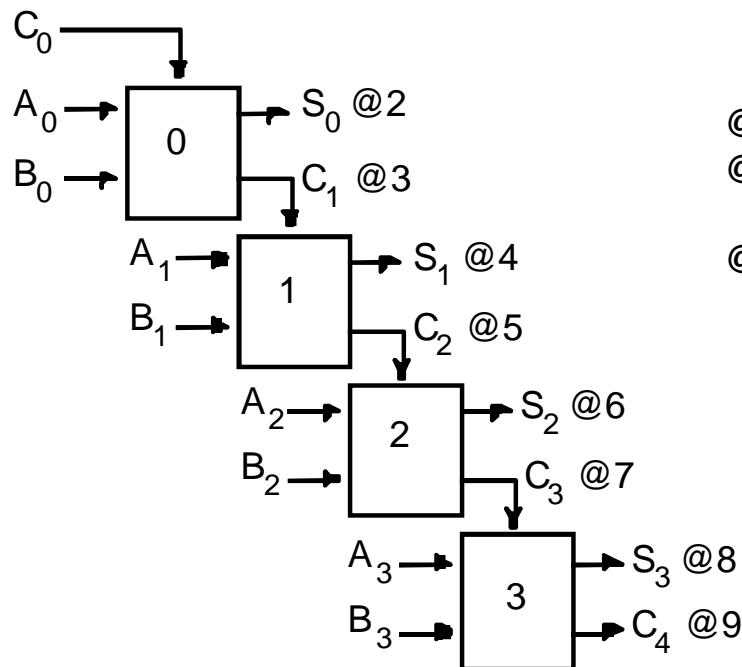

Carry Lookahead Adder

- **Carry Generate**
 - $G_i = A_i B_i$ *must generate carry when $A = B = 1$*
- **Carry Propagate**
 - $P_i = A_i \text{ xor } B_i$ *carry-in will equal carry-out here*
- ***Sum and Carry can be reexpressed in terms of generate/propagate:***

$$S_i = A_i \text{ xor } B_i \text{ xor } C_i = P_i \text{ xor } C_i$$

$$C_{i+1} = A_i B_i + A_i C_i + B_i C_i$$

$$= A_i B_i + C_i (A_i + B_i)$$

$$= A_i B_i + C_i (A_i \text{ xor } B_i)$$

$$= G_i + C_i P_i$$

Carry Lookahead Adder

$$C1 = G0 + P0 C0$$






$$\begin{aligned} C2 &= G1 + P1 C1 \\ &= G1 + P1 (G0 + P0 C0) \\ &= G1 + P1 G0 + P1 P0 C0 \end{aligned}$$

$$\begin{aligned} C3 &= G2 + P2 C2 \\ &= G2 + P2 (G1 + P1 G0 + P1 P0 C0) \\ &= G2 + P2 G1 + P2 P1 G0 + P2 P1 P0 C0 \end{aligned}$$

$$\begin{aligned} C4 &= G3 + P3 C3 \\ &= G3 + P3 G2 + P3 P2 G1 + P3 P2 P1 G0 + P3 P2 P1 P0 C0 \end{aligned}$$

- Each of the carry equations can be implemented in a two-level logic network
- Variables are the adder inputs and carry in to stage 0!



CLA

     

➤ Increasingly complex logic


Delay Analysis of CLA

- C_i 's are generated independent of N

 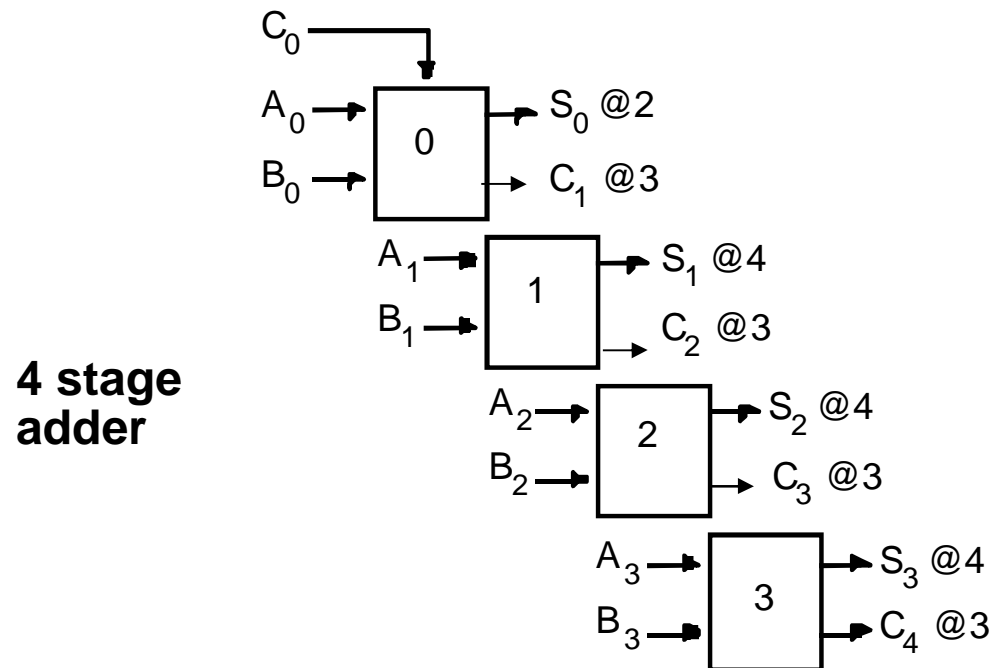


- NOTE: This assumes all gate delay are same.
- Not true, delays depend on fan-ins and fan-out

Cascaded CLA

 


Adder/Subtractor

$$A - B = A + (-B) = A + B' + 1$$

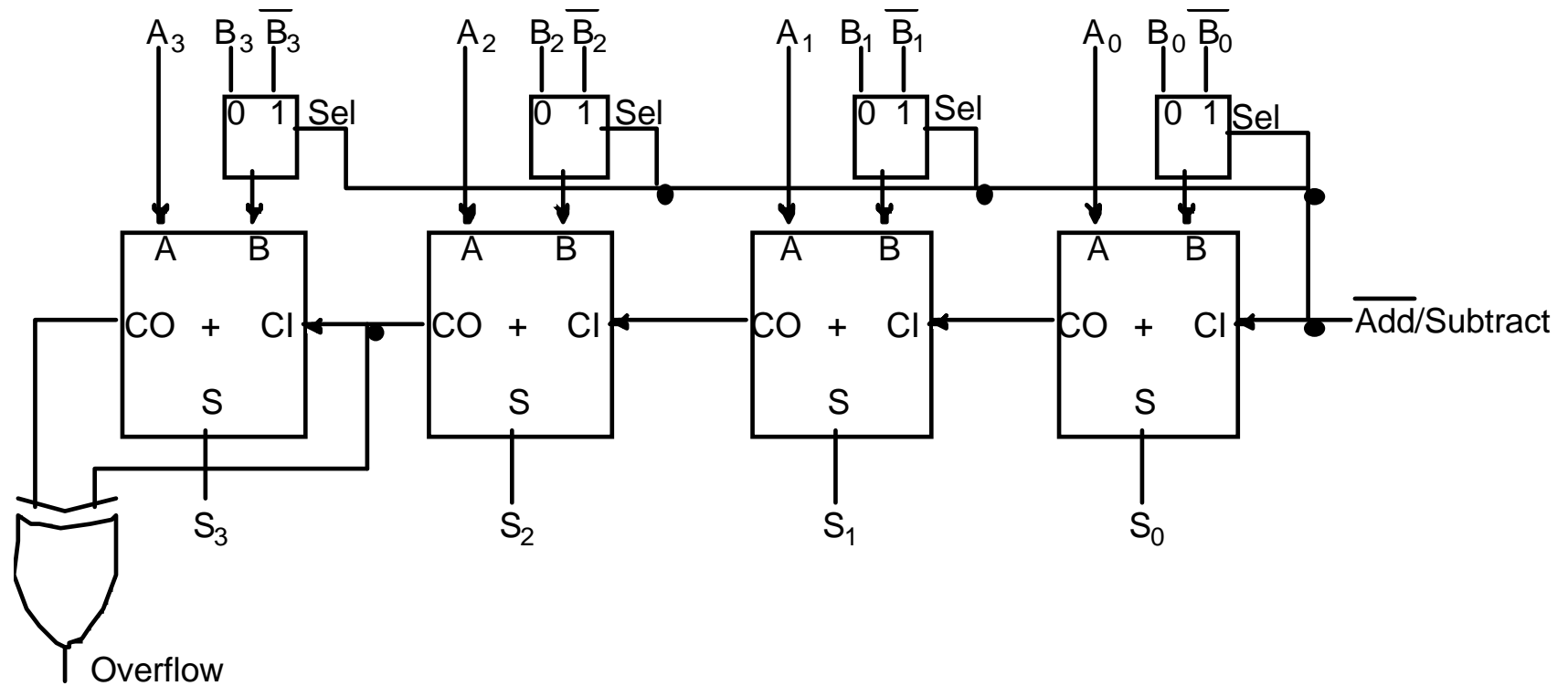


4-bit Binary Adder/Subtractor (cont.)

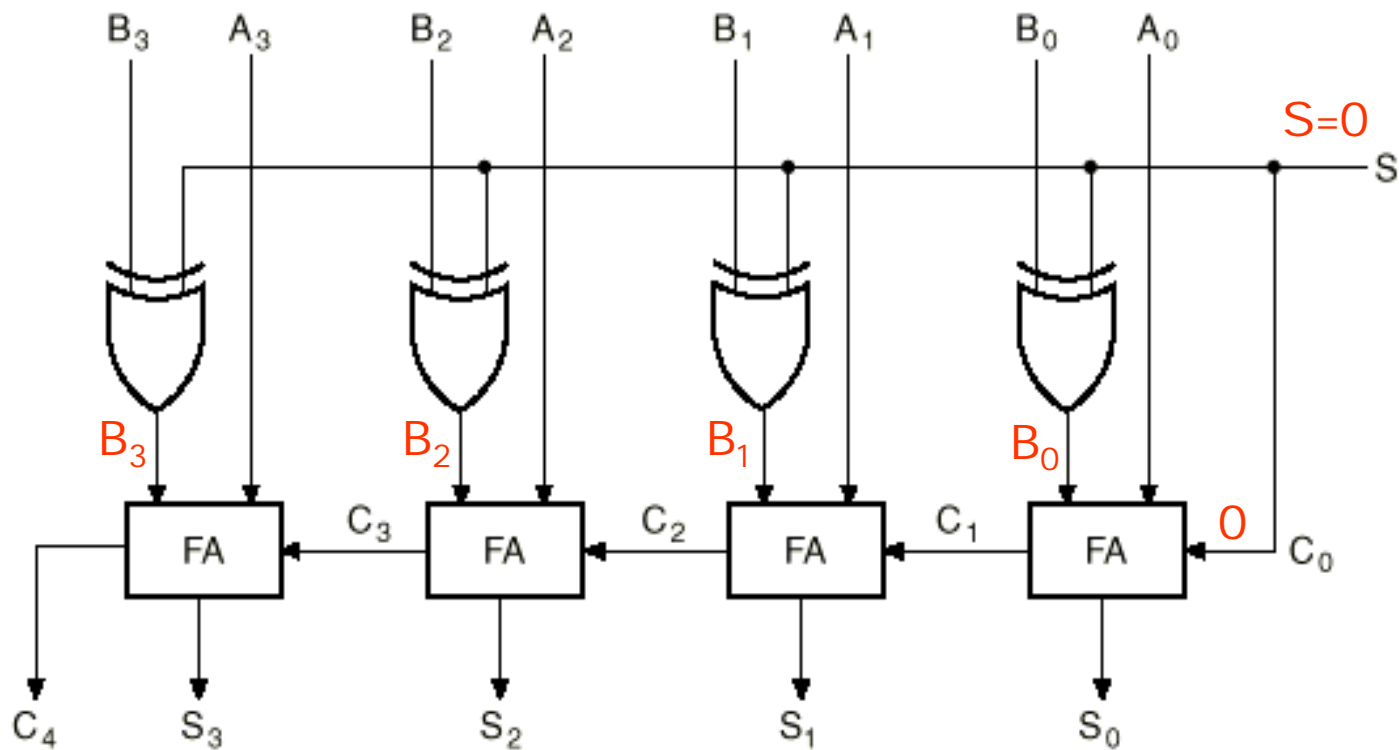

S=0 selects addition

4-bit Binary Adder/Subtractor (cont.)

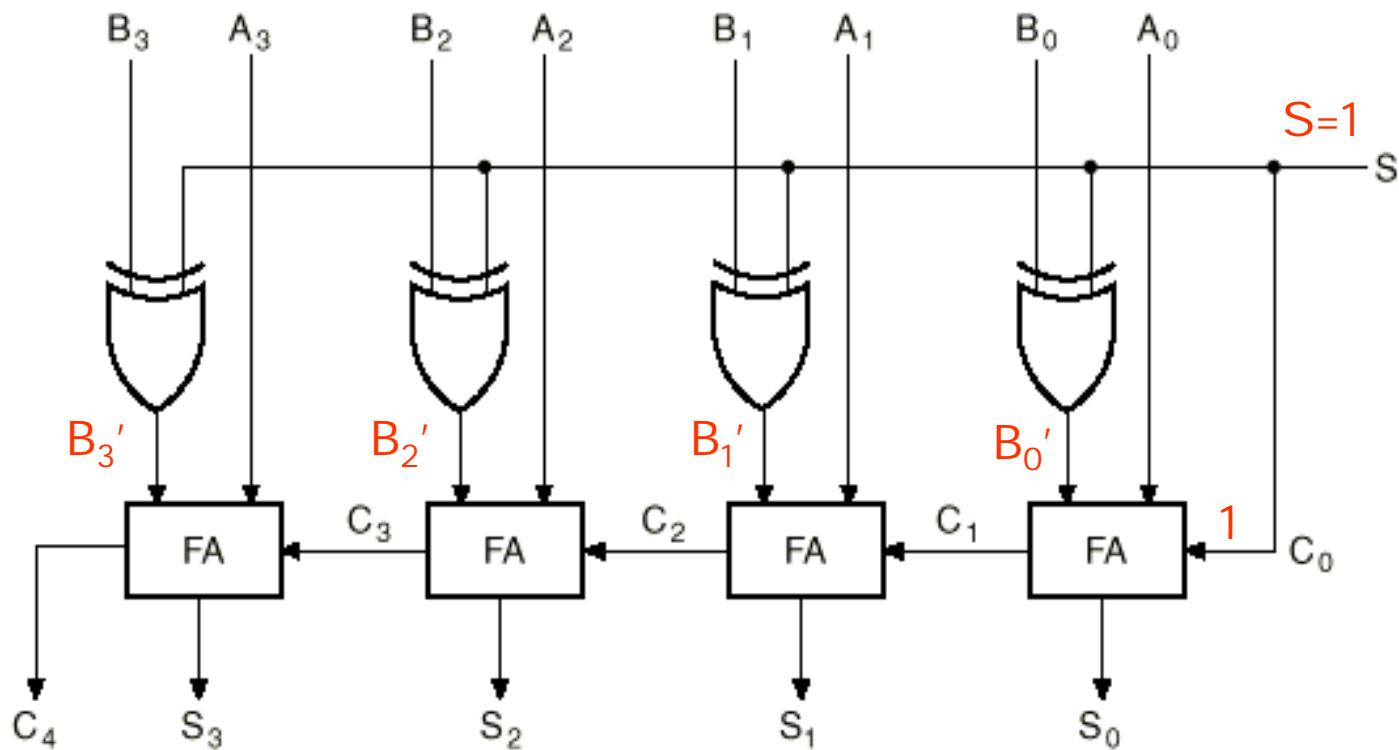

$S=1$ selects subtraction


Overflow

- Overflow can occur ONLY when both numbers have the same sign.
- This condition can be detected when the carry out (C_n) is different than the carry at the previous position (C_{n-1}).

The Overflow problem in Signed-2's Complement (cont.)

 - **Example 1: $M=65_{10}$ and $N=65_{10}$** (In an 8-bit 2's complement system).
 - $M = N = 01000001_2$
 - $M+N = 10000010$ with $C_n=0$. (clearly wrong!)
 - Bring C_n as the MSB to get 010000010_2 (130_{10}) which is correct, but requires 9-bits → overflow occurs.
- **Example 2: $M=-65_{10}$ and $N=-65_{10}$**
 - $M = N = 10111111_2$
 - $M+N = 01111110$ with $C_n=1$. (wrong again!)
 - Bring C_n as the MSB to get 101111110_2 (-130_{10}) which is correct, but also requires 9-bits → overflow occurs.

Overflow Detection in Signed-2's Complement



- $C = 1$ indicates overflow condition when adding/subtr. unsigned numbers.
- $V = 1$ indicates overflow condition when adding/subtr. signed-2's complement numbers


4-Bit ALU

- 74181 TTL ALU

➤ Arithmetic-Logic Unit

Selection				M = 1	M = 0, Arithmetic Functions	
S3	S2	S1	S0	Logic Function	Cn = 0	Cn = 1
0	0	0	0	$F = \text{not } A$	$F = A \text{ minus } 1$	$F = A$
0	0	0	1	$F = A \text{ nand } B$	$F = A B \text{ minus } 1$	$F = A B$
0	0	1	0	$F = (\text{not } A) + B$	$F = A (\text{not } B) \text{ minus } 1$	$F = A (\text{not } B)$
0	0	1	1	$F = 1$	$F = \text{minus } 1$	$F = \text{zero}$
0	1	0	0	$F = A \text{ nor } B$	$F = A \text{ plus } (A + \text{not } B)$	$F = A \text{ plus } (A + \text{not } B) \text{ plus } 1$
0	1	0	1	$F = \text{not } B$	$F = A B \text{ plus } (A + \text{not } B)$	$F = A B \text{ plus } (A + \text{not } B) \text{ plus } 1$
0	1	1	0	$F = A \text{ xnor } B$	$F = A \text{ minus } B \text{ minus } 1$	$F = (A + \text{not } B) \text{ plus } 1$
0	1	1	1	$F = A + \text{not } B$	$F = A + \text{not } B$	$F = A \text{ minus } B$
1	0	0	0	$F = (\text{not } A) B$	$F = A \text{ plus } (A + B)$	$F = (A + \text{not } B) \text{ plus } 1$
1	0	0	1	$F = A \text{ xor } B$	$F = A \text{ plus } B$	$F = A \text{ plus } (A + B) \text{ plus } 1$
1	0	1	0	$F = B$	$F = A (\text{not } B) \text{ plus } (A + B)$	$F = A (\text{not } B) \text{ plus } (A + B) \text{ plus } 1$
1	0	1	1	$F = A + B$	$F = (A + B)$	$F = (A + B) \text{ plus } 1$
1	1	0	0	$F = 0$	$F = A$	$F = A \text{ plus } A \text{ plus } 1$
1	1	0	1	$F = A (\text{not } B)$	$F = A B \text{ plus } A$	$F = A B \text{ plus } A \text{ plus } 1$
1	1	1	0	$F = A B$	$F = A (\text{not } B) \text{ plus } A$	$F = A (\text{not } B) \text{ plus } A \text{ plus } 1$
1	1	1	1	$F = A$	$F = A$	$F = A \text{ plus } 1$

4-Bit ALU

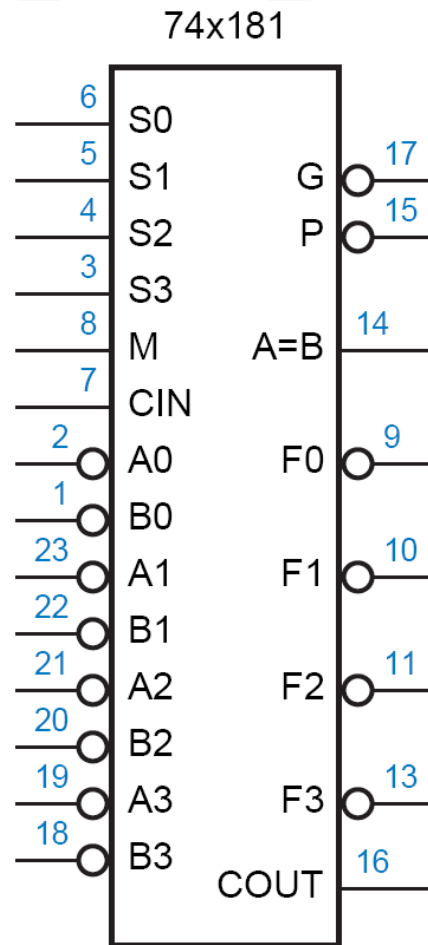

BCD Addition

Addition:

$$5 = 0101$$

$$3 = \underline{0011}$$

$$1000 = 8$$

$$5 = 0101$$

$$8 = \underline{1000}$$

$$1101 = 13!$$

**Problem
when digit
sum exceeds 9**

Solution: add 6 (0110) if sum exceeds 9!

$$5 = 0101$$

$$8 = \underline{1000}$$

$$1101$$

$$6 = \underline{0110}$$

$$1\ 0011 = 1\ 3 \text{ in BCD}$$

$$9 = 1001$$

$$7 = \underline{0111}$$

$$1\ 0000 = 16 \text{ in binary}$$

$$6 = \underline{0110}$$


$$1\ 0110 = 1\ 6 \text{ in BCD}$$

اعداد در مبناهای مختلف

Decimal (base 10)	Binary (base 2)	Octal (base 8)	Hexadecimal (base 16)
00	0000	00	0
01	0001	01	1
02	0010	02	2
03	0011	03	3
04	0100	04	4
05	0101	05	5
06	0110	06	6
07	0111	07	7
08	1000	10	8
09	1001	11	9
10	1010	12	A
11	1011	13	B
12	1100	14	C
13	1101	15	D
14	1110	16	E
15	1111	17	F

Add 0110 to sum whenever it exceeds 1001 (11XX or 1X1X)

BCD Adder

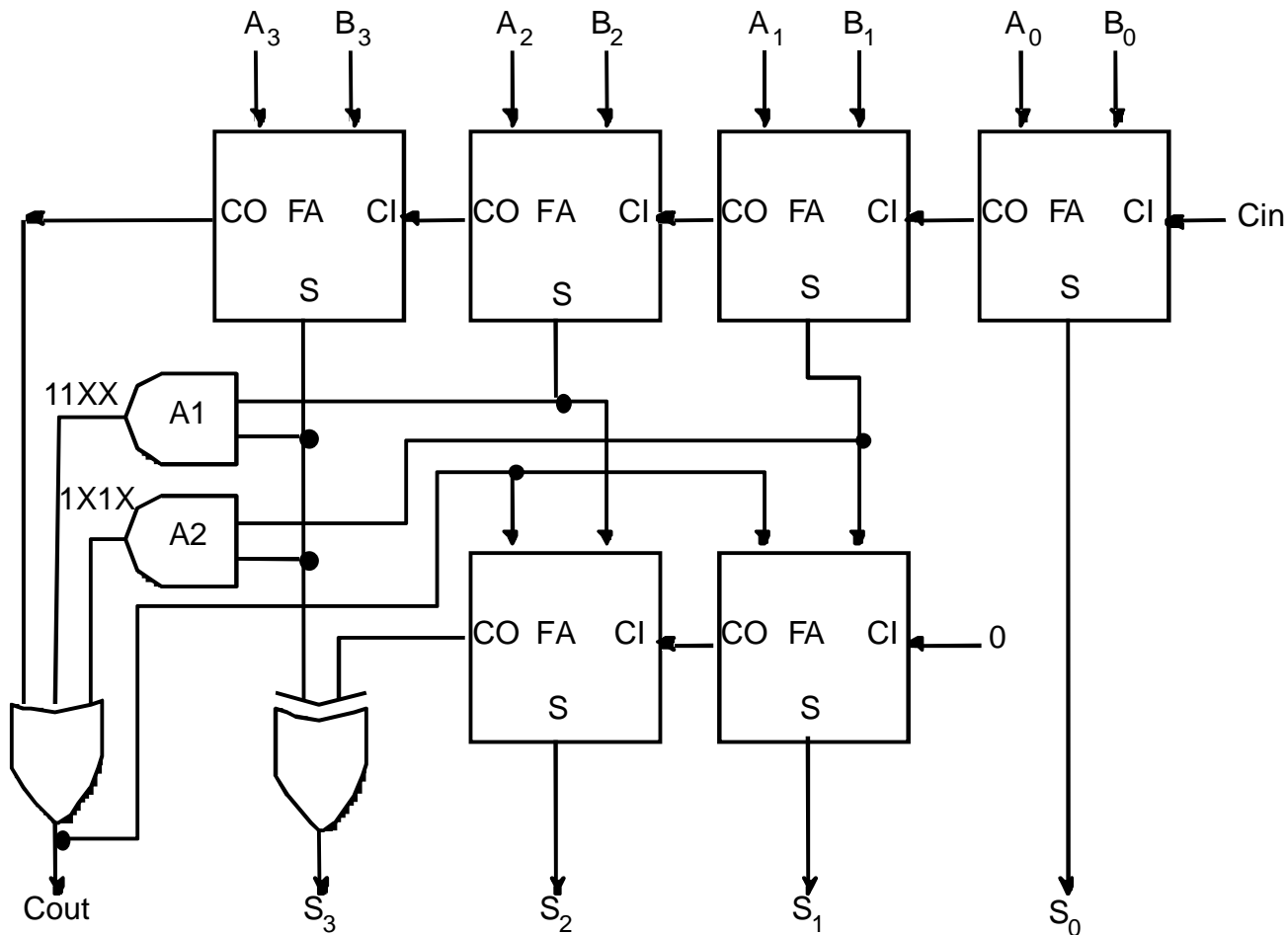

Add 0110 to sum whenever it exceeds 1001 (11XX or 1X1X)