

# Read-Only Memory


## ROM

# ROM

- **Can be used:**
  - to implement any arbitrary combinational circuit
  - as a memory
- **Consists of:**
  - an  $n$ -to- $2^n$  decoder that produces ALL minterms
  - a set of programmable OR gates that produce SoP's
- **Is usually described in terms of:**
  - size of its decoder output (number of memory rows)
  - number of OR gates (memory width)
  - i.e.,  $2^n \times w$ , e.g., 8x4, 1024x8, etc.

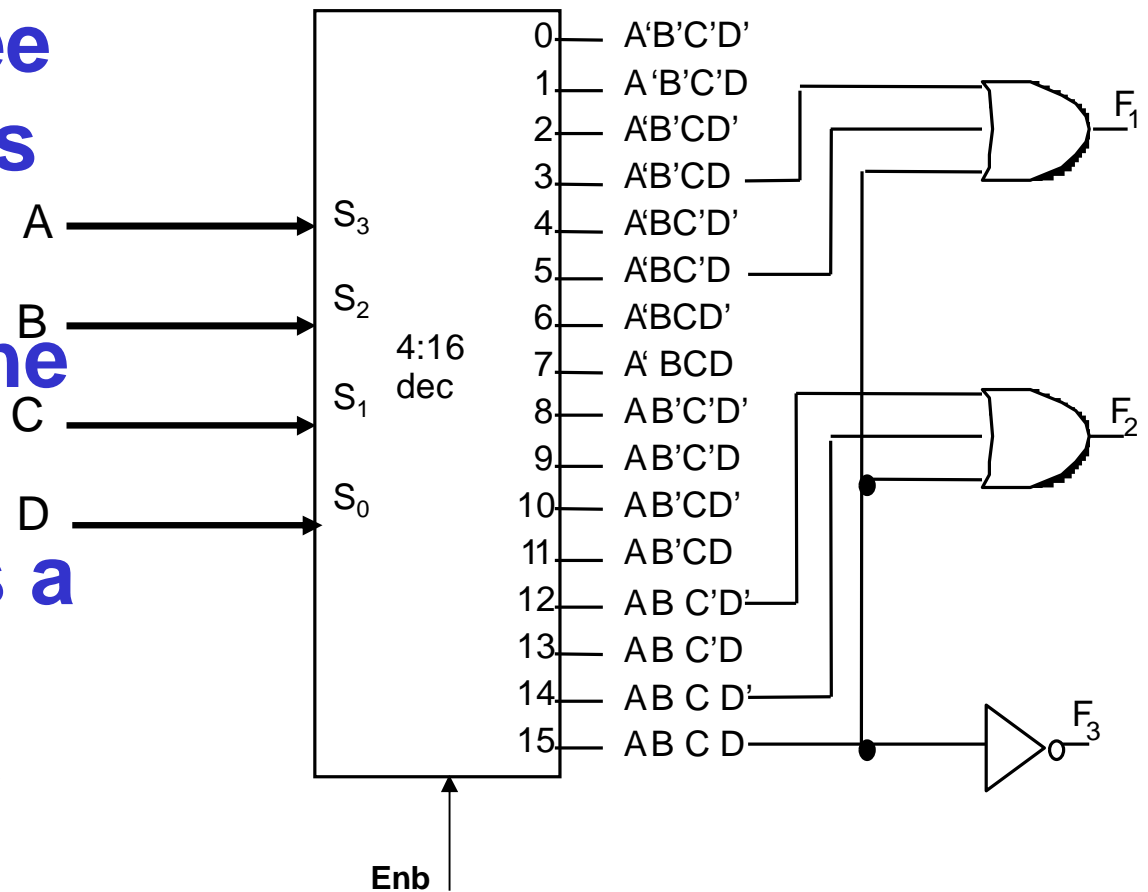
# ROM: Example 1

- A 4-to-16 decoder
- Three OR gates
- Implemented three Boolean functions
- Has an “enable” input to control the output
- Can be viewed as a 16 x 3 memory
- Memory content?



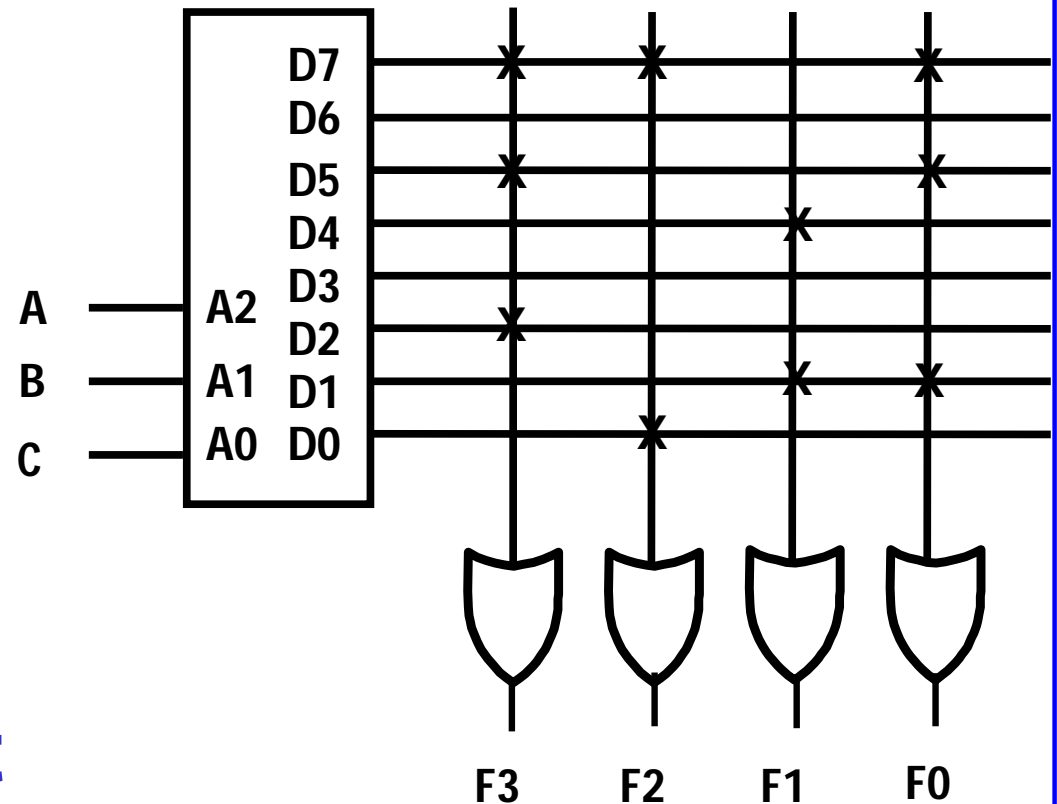
## ROM: Example 2


- A 3-to-8 decoder
- Four OR gates
- Can implement four Boolean functions
- Can be viewed as a 8 x 4 memory
- No “enable” input
- Memory content?




# ROM vs. PLA/PAL

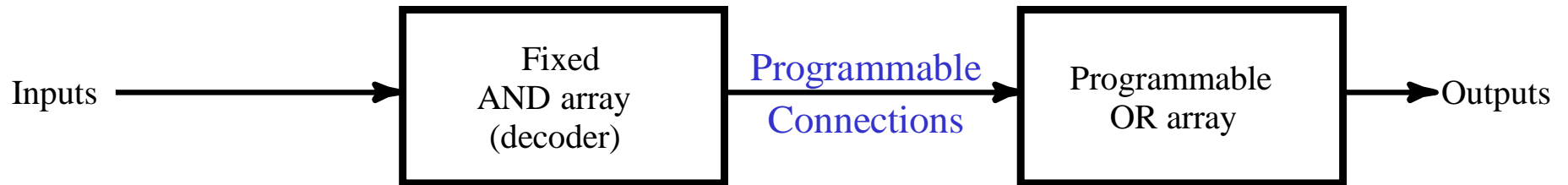

(a) Programmable read-only memory (PROM)

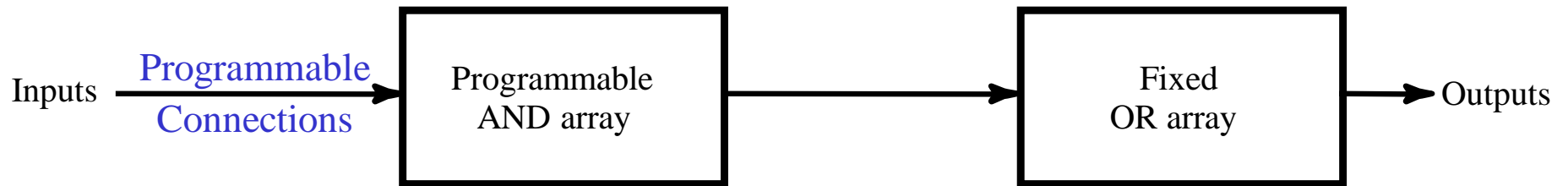

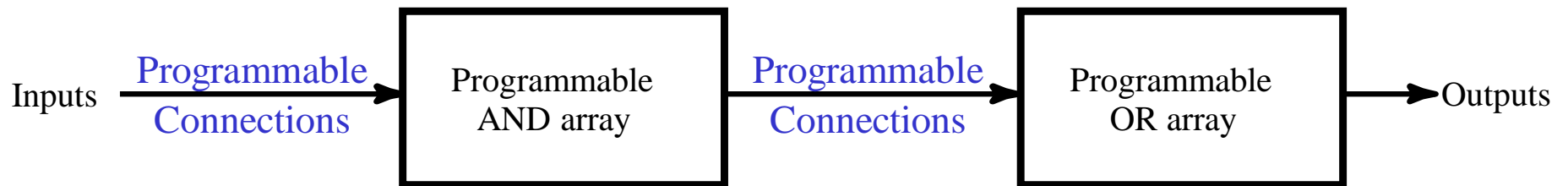(b) Programmable array logic (PAL) device




(c) Programmable logic array (PLA) device

# ROM as a Memory

- ROM's can be viewed as memory with the inputs as address lines, and outputs as the stored data
- Usually have:
  - N input lines,
  - M output lines,
  - Provide  $2^N \times M$  bits of memory
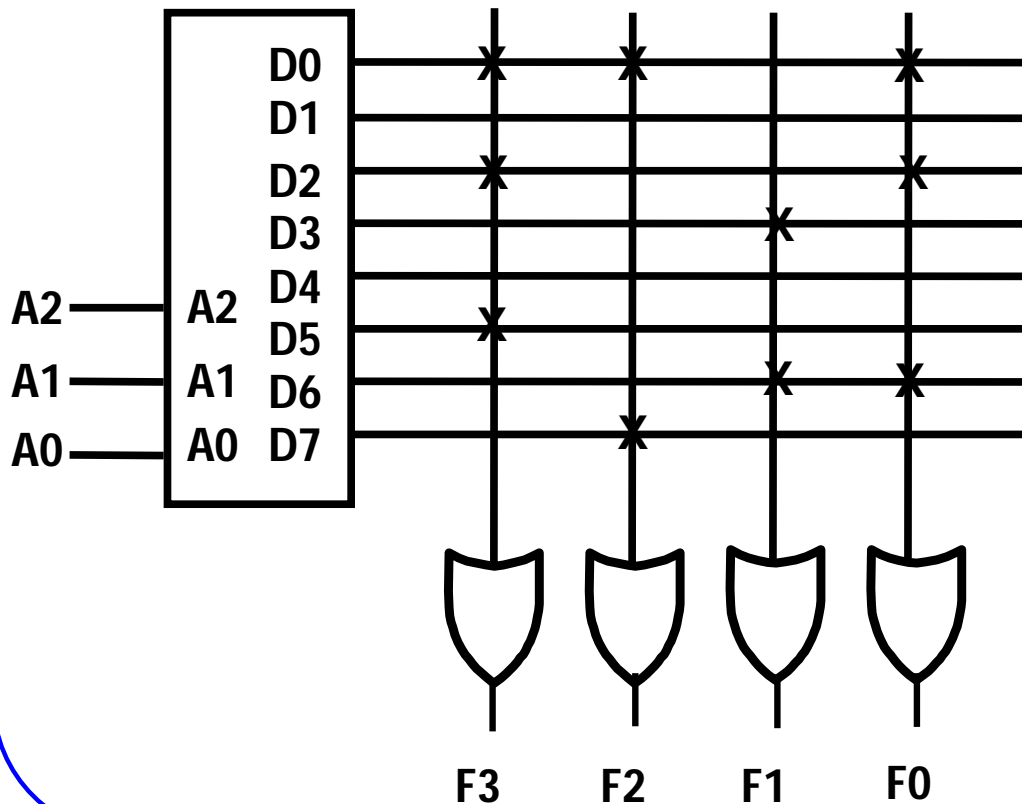
# ROM as Memory (Example)

- **Read Example:** For input  $(A_2, A_1, A_0) = 011$ , output is  $(F_3, F_2, F_1, F_0) = 0010$ .
- What are functions  $F_3$ ,  $F_2$ ,  $F_1$  and  $F_0$  in terms of  $(A_2, A_1, A_0)$ ?



Address	8x4 ROM			
0	1	1	0	1
1	0	0	0	0
2	1	0	0	1
3	0	0	1	0
4	0	0	0	0
5	1	0	0	0
6	0	0	1	1
7	0	1	0	0

# (Memories)

- **Volatile:**

- Random Access Memory (RAM):
  - SRAM: "static"
  - DRAM: "dynamic"

- **Non-Volatile:**

- ROM
- PROM
- EPROM
- EEPROM
- FLASH memory: similar to EEPROM with programmer integrated on chip